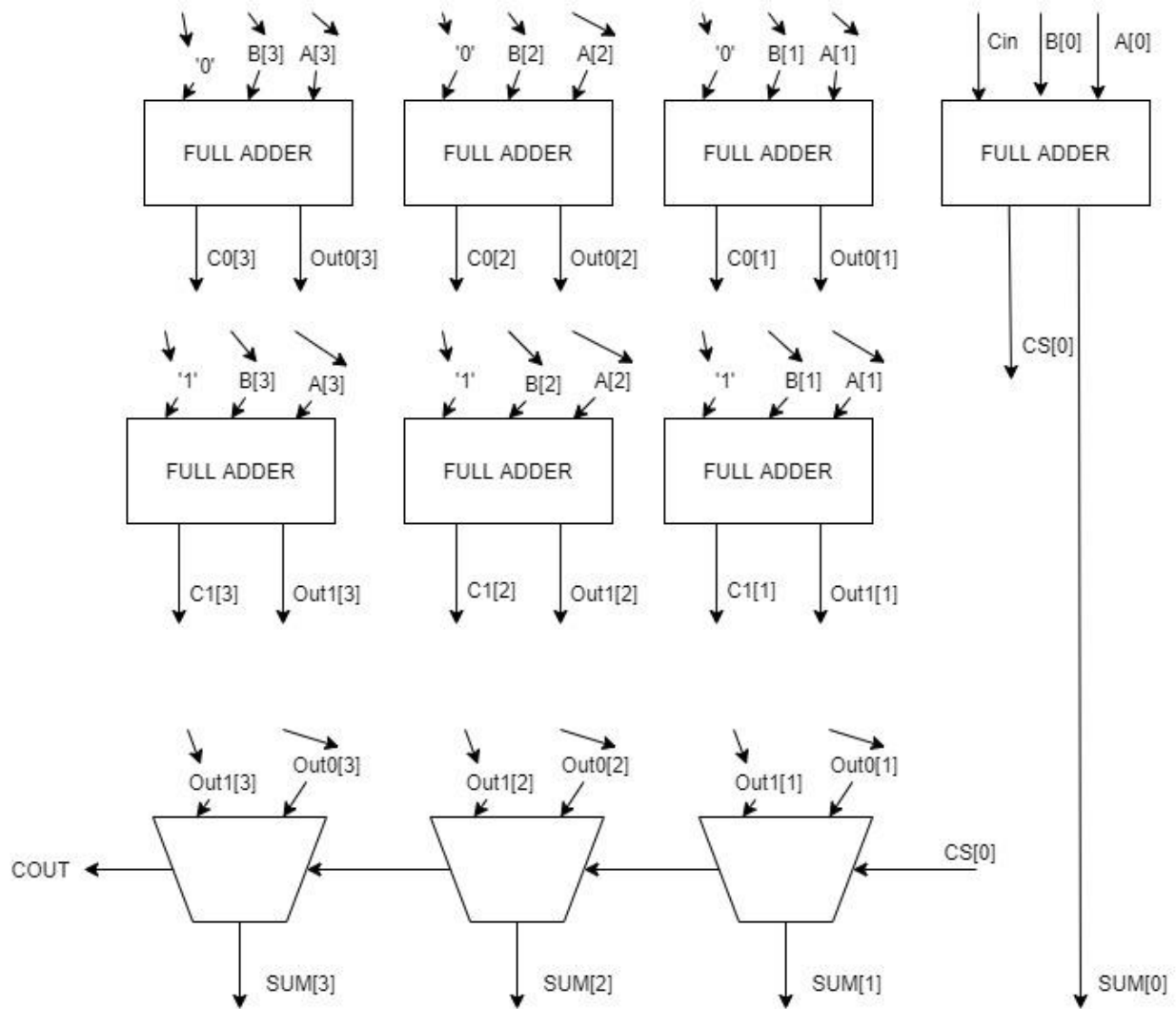# Conditional Sum Adder:

Conditional sum for 4_bits